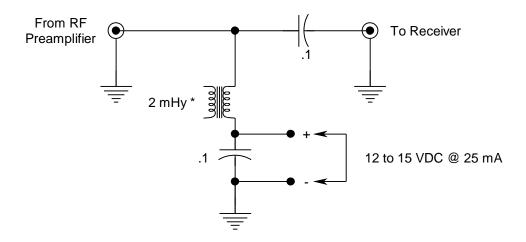
## Power Injector for RF Preamplifier for "TreeTenna" by W5JGV 14 Sept 2007



## **CIRCUIT NOTES:**

- 1) \*Common Mode RF Choke from small switching power supply. Only one winding is used, do NOT short the other winding.
- 2) Unit is built inside a steel electrical junction box.
- 3) Power supply should be hum-free and not exceed 15 volts.